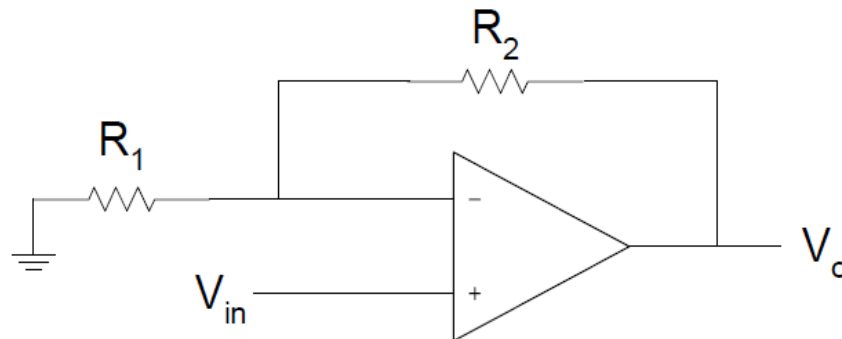


1- For Figure Shown, if the open-loop gain is finite,
(a) Show that the closed-loop gain is given by the expression shown in the Equation given.


$$\frac{V_o}{V_{in}} = - \frac{(1 + R_2/R_1)}{1 + (1 + R_2/R_1)/A}$$

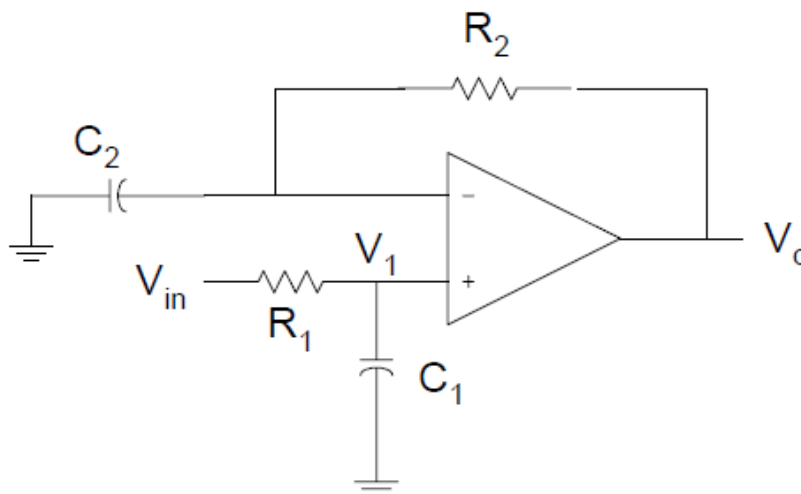(b) If $R_2 = 100\text{K Ohms}$ and $R_1 = 0.5\text{K Ohms}$, plot the percentage error in the magnitude of the closed-loop gain for open-loop gains of 10^2 , 10^4 , 10^6 and 10^8 .



2- For the figure shown:

- Derive the transfer function.
- Use MATLAB to find the poles and zeros.
- Plot the magnitude and phase response, assume that $C_1 = 0.1\mu\text{F}$, $C_2 = 1000\text{ }0.1\mu\text{F}$, $R_1 = 10\text{K Ohms}$, and $R_2 = 10\text{ Ohms}$.



3- An op amp has an open-loop dc gain of 10^7 , the unity gain bandwidth of 10^8 Hz . For an op amp connected in an inverting configuration Figure, plot the magnitude response of the closed-loop gain. If $R_2/R_1 = 100$, 600, 1100.

